

4

Transient Analysis

- 4.1 A $10\ \Omega$ resistor, a 1 H inductor and $1\ \mu\text{F}$ capacitor are connected in parallel. The combination is driven by a unit step current. Under the steady state condition, the source current flows through :
- the resistor
 - the inductor
 - the capacitor only
 - all the three elements
- [1989 : 2 Marks]

- 4.2 If the Laplace transform of the voltage across a capacitor of value of $\frac{1}{2}\text{ F}$ is


$$V_C(s) = \frac{s+1}{s^3+s^2+s+1}$$

the value of the current through the capacitor at $t = 0^+$ is

- 0 A
- 2 A
- $(1/2)\text{ A}$
- 1 A

[1989 : 2 Marks]

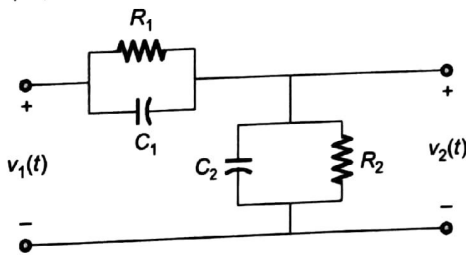- 4.3 For the compensated attenuator of figure, the impulse response under the condition $R_1C_1 = R_2C_2$ is



- $\frac{R_2}{R_1 + R_2} [1 - e^{-\frac{t}{R_1C_1}}] u(t)$
- $\frac{R_2}{R_1 + R_2} \delta(t)$
- $\frac{R_2}{R_1 + R_2} u(t)$
- $\frac{R_2}{R_1 + R_2} e^{-\frac{t}{R_1C_1}} u(t)$


[1992 : 2 Marks]

- 4.4 A ramp voltage, $v(t) = 100t$ Volts, is applied to an RC differentiating circuit with $R = 5\text{ k}\Omega$ and $C = 4\ \mu\text{F}$. The maximum output voltage is

- 0.2 volt
- 2.0 volts
- 10.0 volts
- 50.0 volts

[1994 : 1 Mark]

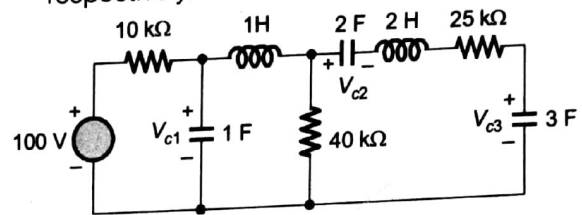
- 4.5 The voltage V_{C1} , V_{C2} and V_{C3} across the capacitors in the circuit in Fig., under steady state, are respectively.



- 80 V, 32 V, 48 V
- 80 V, 48 V, 32 V
- 20 V, 8 V, 12 V
- 20 V, 12 V, 8 V

[1996 : 2 Marks]

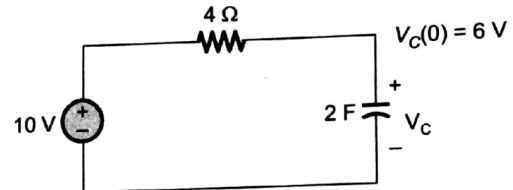
- 4.6 In the circuit of Fig. the energy absorbed by the $4\ \Omega$ resistor in the time interval $(0, \infty)$ is



- 36 Joules
- 16 Joules
- 256 Joules
- None of the above

[1997 : 2 Marks]

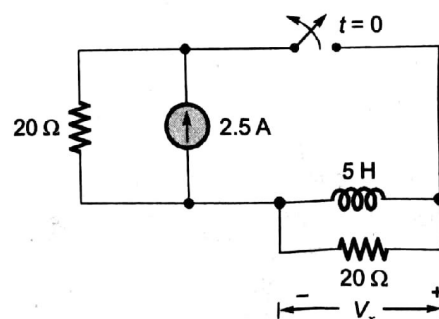- 4.7 In the figure, the switch was closed for a long time before opening at $t = 0$. The voltage V_x at $t = 0^+$ is




- 25 V
- 50 V
- 50 V
- 0 V

[2002 : 1 Mark]

The circuit for 4.8 and 4.9 is given. Assume that the switch S is in position 1 for a long time and thrown to position 2 at $t = 0$.

4.8 At $t = 0^+$, the current i_1 is

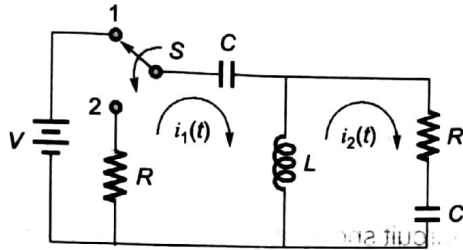

- (a) $-\frac{V}{2R}$ (b) $-\frac{V}{R}$
(c) $-\frac{V}{4R}$ (d) zero

[2003 : 2 Marks]

4.9 $I_1(s)$ and $I_2(s)$ are the Laplace transforms of $i_1(t)$ and $i_2(t)$ respectively. The equations for the loop currents $I_1(s)$ and $I_2(s)$ for the circuit shown in the figure, after the switch is brought from position 1 to position 2 at $t = 0$, are

(a)
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{V}{s} \\ 0 \end{bmatrix}$$



(b)
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{V}{s} \\ 0 \end{bmatrix}$$

(c)
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + Ls + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} -\frac{V}{s} \\ 0 \end{bmatrix}$$

(d)
$$\begin{bmatrix} R + Ls + \frac{1}{Cs} & -Ls \\ -Ls & R + Ls + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} \frac{V}{s} \\ 0 \end{bmatrix}$$


[2003 : 2 Marks]

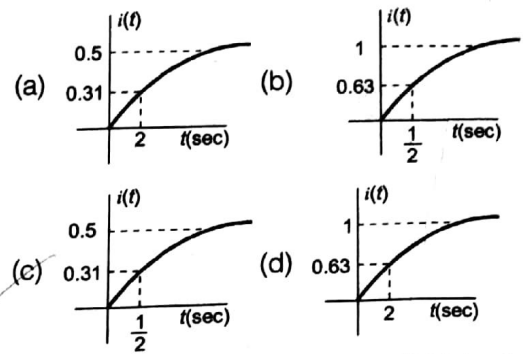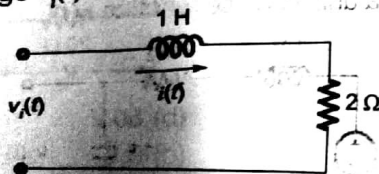4.10 For the R - L circuit shown in the figure, the input voltage $v_i(t) = u(t)$. The current $i(t)$ is



[2004 : 1 Mark]

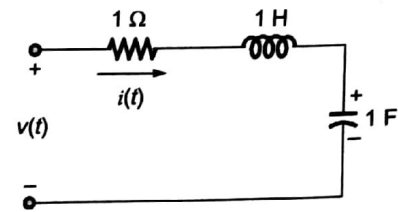
4.11 The circuit shown in the figure has initial current $i_L(0^-) = 1$ A through the inductor and an initial voltage $v_C(0^-) = -1$ V across the capacitor. For input $v(t) = u(t)$, the Laplace transform of the current $i(t)$ for $t \geq 0$ is



- (a) $\frac{s}{s^2 + s + 1}$ (b) $\frac{s + 2}{s^2 + s + 1}$
(c) $\frac{s - 2}{s^2 + s - 1}$ (d) $\frac{s - 2}{s^2 + s + 1}$

[2004 : 2 Marks]

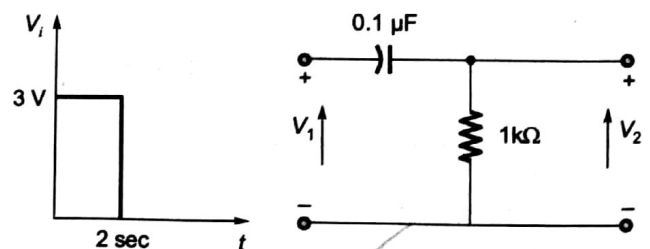
4.12 A square pulse of 3 volts amplitude is applied to C-R circuit shown in the figure. The capacitor is initially uncharged. The output voltage V_2 at time $t = 2$ sec is



- (a) 3 V (b) -3 V
(c) 4 V (d) -4 V

[2005 : 2 Marks]

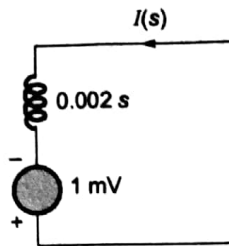
4.13 A 2 mH inductor with some initial current can be represented as shown below, where s is the Laplace Transform variable. The value of initial current is



- (a) 0.5 A (b) 2.0 A
(c) 1.0 A (d) 0.0 A

[2006 : 1 Mark]

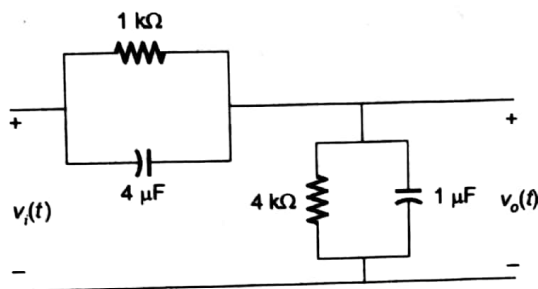
- 4.14 In the figure shown below, assume that all the capacitors are initially uncharged. If $v_i(t) = 10u(t)$ Volts, $v_o(t)$ is given by



- (a) $8e^{-t/0.004}$ Volts
(b) $8(1 - e^{-t/0.004})$ Volts
(c) $8u(t)$ Volts
(d) 8 Volts

[2006 : 1 Mark]

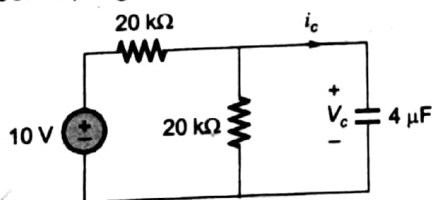
- 4.15 In the circuit shown, V_C is 0 volts at $t = 0$ sec. For $t > 0$, the capacitor current $i_c(t)$, where t is in seconds, is given by



- (a) $0.50 \exp(-25t)$ mA
(b) $0.25 \exp(-25t)$ mA
(c) $0.50 \exp(-12.5t)$ mA
(d) $0.25 \exp(-6.25t)$ mA


[2007 : 2 Marks]

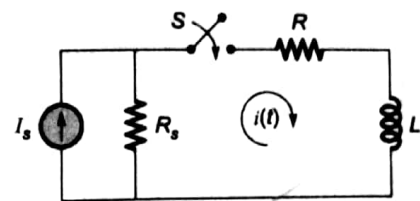- 4.16 In the following circuit, the switch S is closed at $t = 0$. The rate of change of current $\frac{di}{dt}(0^+)$ is given by



- (a) 0 (b) $\frac{R_s I_s}{L}$
(c) $\frac{(R + R_s) I_s}{L}$ (d) ∞ [2008 : 1 Mark]

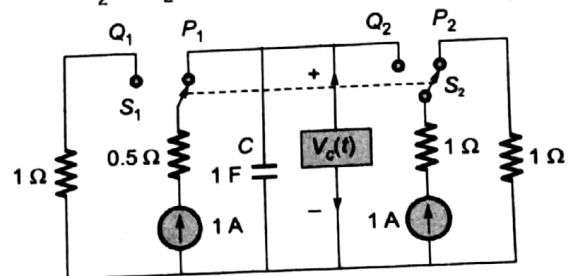- 4.17 The circuit shown in the figure is used to charge the capacitor C alternately from two current sources as indicated. The switches S_1 and S_2 are mechanically coupled and connected as follows: For $2nT \leq t < (2n+1)T$, ($n = 0, 1, 2, \dots$) S_1 to P_1 and S_2 to P_2 . For $(2n+1)T \leq t < (2n+2)T$, ($n = 0, 1, 2, \dots$) S_1 to Q_1 and S_2 to Q_2 .




Assume that the capacitor has zero initial charge. Given that $u(t)$ is a unit step function, the voltage $V_C(t)$ across the capacitor is given by

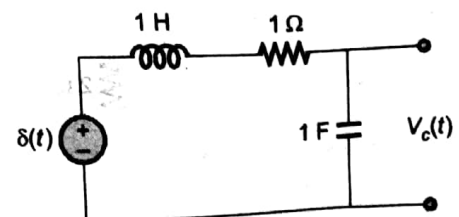- (a) $\sum_{n=0}^{\infty} (-1)^n tu(t - nT)$
(b) $u(t) + 2 \sum_{n=1}^{\infty} (-1)^n u(t - nT)$
(c) $tu(t) + 2 \sum_{n=1}^{\infty} (-1)^n (t - nT)u(t - nT)$
(d) $\sum_{n=0}^{\infty} [0.5 - e^{-(t-2nT)} + 0.5e^{-(t-2nT-T)}]$

[2008 : 2 Marks]

Common Data for Questions 4.18 and 4.19: The following series RLC circuit with zero initial conditions is excited by a unit impulse function $\delta(t)$.



4.18 For $t > 0$, the output voltage $V_o(t)$ is

- (a) $\frac{2}{\sqrt{3}} \left(e^{-\frac{1}{2}t} - e^{-\frac{\sqrt{3}}{2}t} \right)$
- (b) $\frac{2}{\sqrt{3}} t e^{-\frac{1}{2}t}$
- (c) $\frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t\right)$
- (d) $\frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t\right)$


[2008 : 2 Marks]

4.19 For $t > 0$, the voltage across the resistor is

- (a) $\frac{1}{\sqrt{3}} \left(e^{-\frac{\sqrt{3}}{2}t} - e^{-\frac{1}{2}t} \right)$
- (b) $e^{-\frac{1}{2}t} \left[\cos\left(\frac{\sqrt{3}}{2}t\right) - \frac{1}{\sqrt{3}} \sin\left(\frac{\sqrt{3}}{2}t\right) \right]$
- (c) $\frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \sin\left(\frac{\sqrt{3}}{2}t\right)$
- (d) $\frac{2}{\sqrt{3}} e^{-\frac{1}{2}t} \cos\left(\frac{\sqrt{3}}{2}t\right)$

[2008 : 2 Marks]

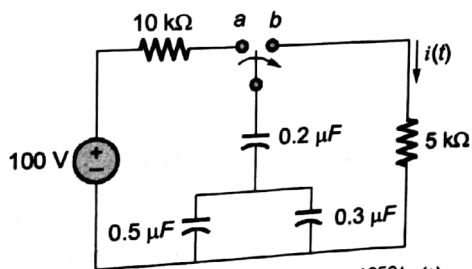4.20 The switch in the circuit shown was on position a for a long time, and is moved to position b at time $t = 0$. The current $i(t)$ for $t > 0$ is given by



- (a) $0.2e^{-125t}u(t)$ mA
- (b) $20e^{-1250t}u(t)$ mA
- (c) $0.2e^{-1250t}u(t)$ mA
- (d) $20e^{-1000t}u(t)$ mA

[2009 : 2 Marks]

4.21 The time domain behaviour of an RL circuit is represented by


$$L \frac{di}{dt} + Ri = V_0 (1 + Be^{-Rt/L} \sin t) u(t)$$

For an initial current of $i(0) = \frac{V_0}{R}$, the steady state value of the current is given by

- (a) $i(t) \rightarrow \frac{V_0}{R}$
- (b) $i(t) \rightarrow \frac{2V_0}{R}$
- (c) $i(t) \rightarrow \frac{V_0}{R}(1+B)$
- (d) $i(t) \rightarrow \frac{2V_0}{R}(1+B)$

[2009 : 2 Marks]

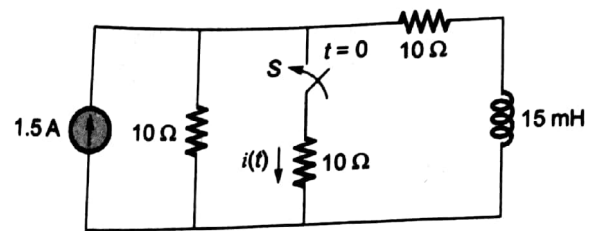
4.22 In the circuit shown, the switch S is open for a long time and is closed at $t = 0$. The current $i(t)$ for $t \geq 0^+$ is



- (a) $i(t) = 0.5 - 0.125e^{-1000t}$ A
- (b) $i(t) = 1.5 - 0.125e^{-1000t}$ A
- (c) $i(t) = 0.5 - 0.5e^{-1000t}$ A
- (d) $i(t) = 0.375e^{-1000t}$ A

[2010 : 2 Marks]

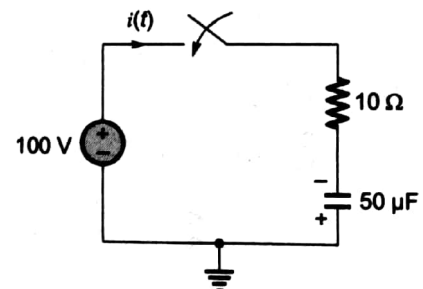
4.23 In the circuit shown below, the initial charge on the capacitor is 2.5 mC, with the voltage polarity as indicated. The switch is closed at time $t = 0$. The current $i(t)$ at a time t after the switch is closed is



- (a) $i(t) = 15 \exp(-2 \times 10^3 t)$ A
- (b) $i(t) = 5 \exp(-2 \times 10^3 t)$ A
- (c) $i(t) = 10 \exp(-2 \times 10^3 t)$ A
- (d) $i(t) = -5 \exp(-2 \times 10^3 t)$ A

[2011 : 2 Marks]

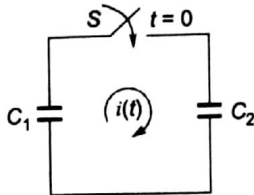4.24 In the following figure, C_1 and C_2 are ideal capacitors. C_1 had been charged to 12 V before the ideal switch S is closed at $t = 0$. The current $i(t)$ for all t is



- (a) zero
(b) a step function
(c) an exponentially decaying function
(d) an impulse function


[2012 : 1 Mark]

4.25 For maximum power transfer between two cascaded sections of an electrical network, the relationship between the output impedance Z_1 of the first section to the input impedance Z_2 of the second section is

- (a) $Z_2 = Z_1$ (b) $Z_2 = -Z_1$
(c) $Z_2 = Z_1^*$ (d) $Z_2 = -Z_1^*$


[2014 : 1 Mark, Set-1]

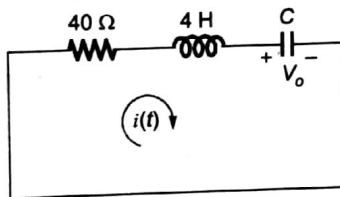4.26 In the circuit shown in the figure, the value of capacitor C (in mF) needed to have critically damped response $i(t)$ is ____.




[2014 : 2 Marks, Set-1]

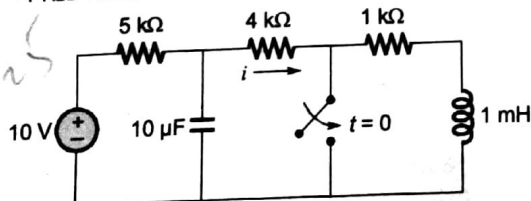4.27 In the figure shown, the ideal switch has been open for a long time. If it is closed at $t = 0$, then the magnitude of the current (in mA) through the $4 \text{ k}\Omega$ resistor at $t = 0^+$ is ____.



[2014 : 1 Mark, Set-2]

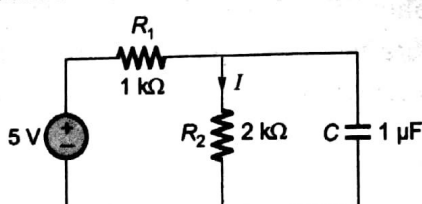4.28 In the figure shown, the capacitor is initially uncharged. Which one of the following expressions describes the current $I(t)$ (in mA) for $t > 0$?



$$(a) I(t) = \frac{5}{3}(1 - e^{-t/\tau}), \tau = \frac{2}{3} \text{ msec}$$


$$(b) I(t) = \frac{5}{2}(1 - e^{-t/\tau}), \tau = \frac{2}{3} \text{ msec}$$

$$(c) I(t) = \frac{5}{3}(1 - e^{-t/\tau}), \tau = 3 \text{ msec}$$

$$(d) I(t) = \frac{5}{2}(1 - e^{-t/\tau}), \tau = 3 \text{ msec}$$


[2014 : 2 Marks, Set-2]

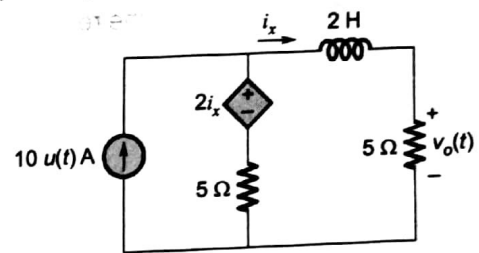4.29 In the circuit shown in the figure, the value of $v_o(t)$ (in volts) for $t \rightarrow \infty$ is ____.



[2014 : 2 Marks, Set-4]

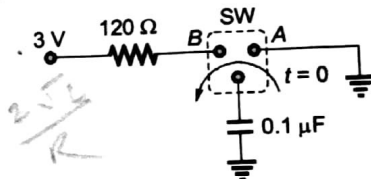
4.30 In the circuit shown, the switch SW is thrown from position A to position B at time $t = 0$. The energy (in μJ) taken from the 3 V source to charge the $0.1 \text{ }\mu\text{F}$ capacitor from 0 V to 3 V is



- (a) 0.3 (b) 0.45
(c) 0.9 (d) 3


[2015 : 1 Mark, Set-1]

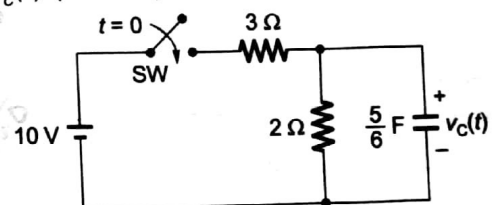4.31 In the circuit shown, switch SW is closed at $t = 0$. Assuming zero initial conditions, the value of $v_c(t)$ (in Volts) at $t = 1 \text{ sec}$ is ____.




[2015 : 2 Marks, Set-1]

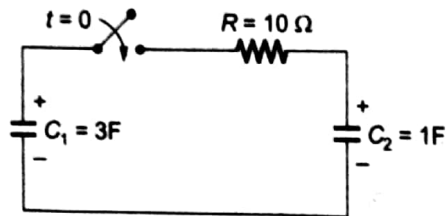4.32 In the circuit shown, the initial voltages across the capacitors C_1 and C_2 are 1 V and 3 V , respectively. The switch is closed at time $t = 0$. The total energy dissipated (in Joules) in the resistor R until steady state is reached, is ____.



[2015 : 2 Marks, Set-2]

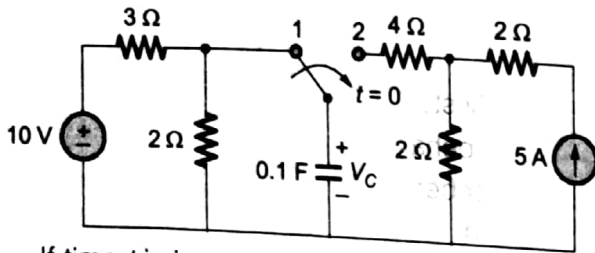- 4.33 The switch has been in position 1 for a long time and abruptly changes to position 2 at $t = 0$.




If time t is in seconds, the capacitor voltage V_C (in volts) for $t > 0$ is given by

- (a) $4(1 - \exp(-t/0.5))$ (b) $10 - 6 \exp(-t/0.5)$
 (c) $4(1 - \exp(-t/0.6))$ (d) $10 - 6 \exp(-t/0.6)$

[2016 : 1 Mark, Set-2]

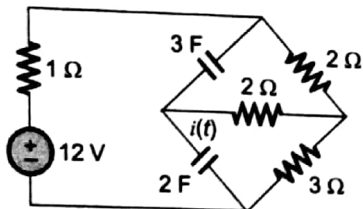- 4.34 Assume that the circuit in the figure has reached the steady state before time $t = 0$ when the 3Ω resistor suddenly burns out, resulting in an open circuit. The current $i(t)$ (in ampere) at $t = 0^+$ is _____.




[2016 : 2 Mark, Set-3]

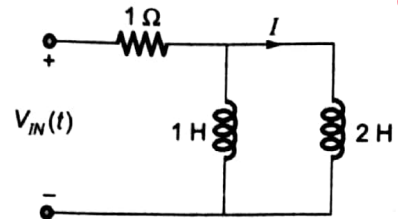- 4.35 In the circuit shown, the voltage $V_{IN}(t)$ is described by:


$$V_{IN}(t) = \begin{cases} 0, & \text{for } t < 0 \\ 15 \text{ Volts,} & \text{for } t \geq 0 \end{cases}$$

where t is in seconds. The time (in seconds) at which the current I in the circuit will reach the value 2 Amperes is _____.



[2017 : 2 Marks, Set-1]

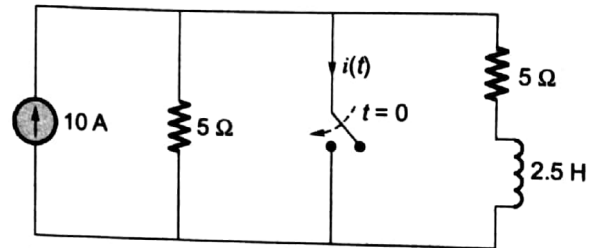- 4.36 The switch in the circuit, shown in the figure, was open for a long time and is closed at $t = 0$.



The current $i(t)$ (in ampere) at $t = 0.5$ seconds is _____.

[2017 : 2 Marks, Set-2]

Answers

- 4.1 (b) 4.2 (c) 4.3 (b) 4.4 (b) 4.5 (b) 4.6 (b) 4.7 (c) 4.8 (a) 4.9 (c)
 4.10 (c) 4.11 (b) 4.12 (b) 4.13 (a) 4.14 (c) 4.15 (a) 4.16 (b) 4.17 (c) 4.18 (d)
 4.19 (b) 4.20 (b) 4.21 (a) 4.22 (a) 4.23 (a) 4.24 (d) 4.25 (c) 4.28 (a) 4.30 (c)
 4.33 (d)